

Computer Systems 1  
Lecture 20

CMOS and VLSI  
How Logic Gates Work

Dr John T. O'Donnell  
School of Computing Science  
University of Glasgow

Copyright © 2019 John T. O'Donnell

# Topics

- Doped silicon
- CMOS technology
- Logic gates
- Integrated circuits
- Dynamic memory

# Doped Silicon

# Physics Background

## ***Atoms***

Electrons have negative charge

Nucleus contains protons with positive charge

- Like charges repel
- Unlike charges attract

# Chemistry Background

- Electron Shells

- The electrons around a nucleus are grouped into shells. Each shell has an ideal number of electrons that will fit into it, and the atom “likes” to have the outer shell filled

- Covalent Chemical Bonds

- Two atoms with partially filled outer shells can “share” some electrons; they bond together

# Insulators and Conductors

- If an atom has just enough electrons to fill the outer shell exactly, then electricity (moving electrons) can't go through it. It's an insulator.
- If an atom has only a few electrons in a big shell far from the nucleus, it's easy to get those electrons moving. It's a conductor (silver, copper, gold, ...)

# Semiconductors

- Silicon is a semiconductor, halfway between an insulator and a conductor.
- Its outer shell wants to have 8 electrons, but the Silicon atom provides only 4.
- The atom forms covalent bonds with its neighbors, ending with filled shells.
- This is a silicon crystal, which is a good insulator

# Doped Silicon

We could take a silicon crystal, but replace a few of the silicon atoms with Boron or Phosphorous.

- This would give us either one more or one fewer electrons in the outer shell
- And that means that an electrical field can more easily get some of those electrons moving, since the outer shell is not completely stable




# N and P Type Silicon


- Pure silicon is an insulator, but it can be doped, turning it into:
  - N type silicon, a semiconductor with negative charge carriers (called free electrons)
  - P type silicon, a semiconductor with positive charge carriers (called holes). *These are spots where an electron would like to be (would lower the energy) but isn't.*

# Negative Charge Carriers

*N type*

 


# Positive Charge Carriers

 


*In reality, the only movable charge carriers are negative electrons. However, they behave as if there are holes that can move, and the holes act as if they have a positive charge.*

# Junctions

 

a **PN junction** is formed when a P-type region is fabricated adjacent to an N-type region

# Forward Biased Junction

 


New hole injected by  
+ power supply

Newly injected  
electron

An electron annihilates a hole, enabling  
further electrons to move left and further  
holes to move right

***Current flows steadily!***

# Reverse Biased Junction

 

***No current flows across the junction!***


There are no free charge carriers near the junction, so it becomes an insulating crystal

# The Junction Diode

A diode allows current to flow across it one direction but not the other

A PN junction does exactly that!

# N-Type Wires

 


*Each of the four N-type wires carries a signal safely; a short circuit is impossible because it would have to cross a reverse biased junction*




# CMOS Technology

# Metal—Oxide—Semiconductor

 

***This is called  
MOS technology***

# Neutral Gate

 


*If the gate is not charged, it has no effect on the substrate*
 
# Positive Gate, P-type Substrate



*Positive  
power supply*

*Free electrons in the substrate  
are attracted to the region  
under the gate, where they are  
stuck because of the insulator*




***If the gate is positively charged, it temporarily transforms part of the P-type substrate into N-type***

# Gap in a Wire

  


*No current can flow between **a** and **b**, in either direction, since it would have to cross a reverse biased junction*

# N-Channel Pass Transistor

 

*A pass transistor consists of a MOS capacitor built right over a gap in a wire*


# Open N-Channel

 

*If the gate is neutral, so that the capacitor is discharged, then current cannot flow between the source and drain, and we just have a wire containing a gap*

*The source and drain are disconnected!*

# Closed N-Channel

 


*If the gate is positive, so the capacitor is charged, then the temporary N-type region under the gate closes the connection.*

*Current flows between source and drain!*



# A Controllable Switch

 

The N-channel pass transistor is a switch controlled by the gate

# P-Channel Pass Transistors

The same design, with the N/P and  $-/+$  polarity reversed, is a P-channel pass transistor


- If the gate is **neutral**, the wire has a gap
- If the gate is **negatively** charged, the source and drain are temporarily connected

# CMOS: Complementary MOS


- A circuit that contains both P-channel and N-channel devices is called CMOS
- Notice that we need both a positive voltage (to control the N-channel transistors) and a negative voltage (to control the P-channel transistors).
- CMOS is currently the dominant technology

# Logic Gates

# N and P Channel Transistors

 

 The **N**-channel transistor makes connection if gate is +




The **P**-channel transistor makes connection if gate is -

# CMOS Inverter

The two logic values are the power supply values,  $+v/2$  and  $-v/2$

$$y = \text{inv } x$$

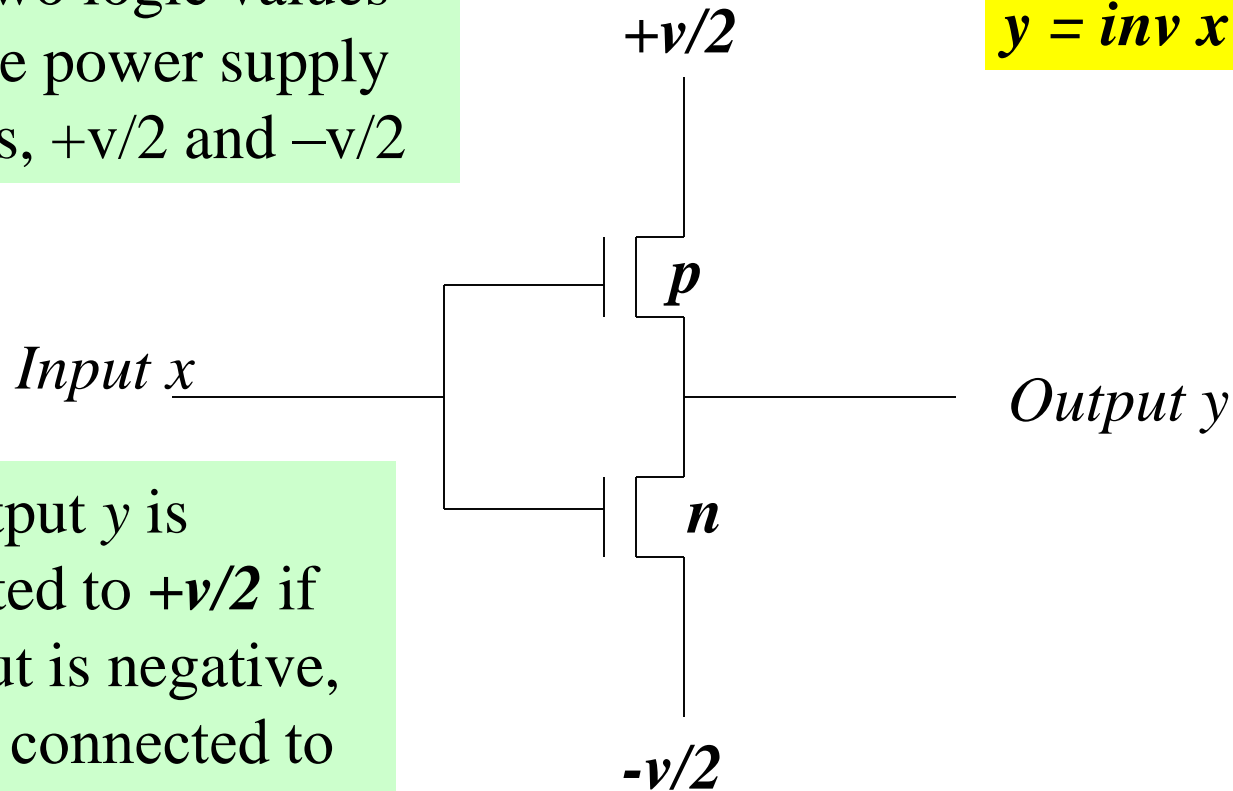

The output  $y$  is connected to  $+v/2$  if the input is negative, and it's connected to  $-v/2$  if the input is positive

# Steering Logic

- Using pass transistors to control what connections are made, without always using conventional logic gates like *and2*, *or2*, *xor2*, *inv* etc.
- These logic gates (*and2* etc.) are actually implemented using steering logic

# Synthesis of Logic Gate Circuits

- The aim: design a circuit that implements a logic function  $f$  taking some inputs  $x, y, \dots$
- The method:
  - Build a network of pass transistors that connect the output to High exactly when  $f(x, y) = \text{True}$
  - Build another network that connects the output to Low exactly when  $f(x, y) = \text{False}$



# Connecting “source” and “drain”

- Suppose  $x$  is on the gate of a transistor
- An **N channel** transistor will connect if  *$x$  is high*
- A **P channel** transistor will connect if  *$x$  is low*

# Basic Steering Functions

- A logical conjunction (**and**) is implemented by transistors in **series**
- A logical disjunction (**or**) is implemented by transistors in **parallel**

# The nor2 logic gate

A 2-input or gate, with the output inverted

a	b	Nor2 a b
0	0	1
0	1	0
1	0	0
1	1	0

# The *nor2* Logic Function

$$z = \text{nor2 } x \ y$$

$$= \text{True iff } \neg (x \vee y) = \neg x \wedge \neg y$$


$$= \text{False iff } x \vee y$$

These two expressions are used directly to construct the steering logic...
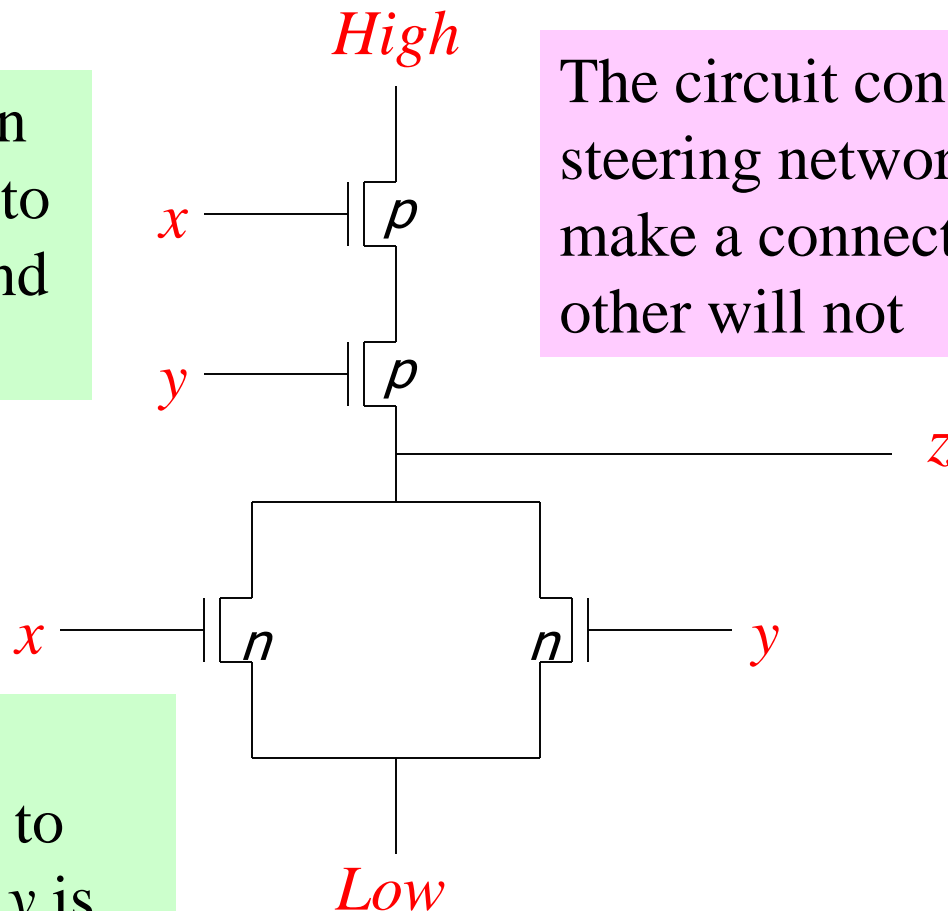
# Implementation of $z = \text{nor2 } x \ y$

The transistors in series connect  $z$  to *High* if both  $x$  and  $y$  are *Low*

The circuit consists of two steering networks: one will make a connection, the other will not



The transistors in parallel connect  $z$  to *Low* if either  $x$  or  $y$  is *High*

# Requirements of a Logic Circuit

- For all inputs, the output must be connected to either High or Low

Otherwise, the output signal is floating – neither True nor False

- There must not be any combination of input values that cause both networks to close

This would connect the High and Low power supplies together, resulting in a short circuit!

# Integrated Circuits

# Integrated Circuits

- We can fabricate many transistors on the same chip of silicon
- We can also fabricate wires connecting them directly on the chip
  - Short wires can simply be N or P type paths that are surrounded by the opposite type
  - Long wires are implemented by placing paths of aluminum on top of the surface



# IC Fabrication

- A photographic process – efficient because all the devices on the chip are manufactured in parallel
- The chip is built up in stages (e.g. doping selected regions to change them from P to N type)
- Photoresist is used to mask off the portions that are to be left unchanged

## Fabricating one layer: doping


- State of the chip: the surface is P-type silicon
- Aim: change some regions (which form wires) to N-type in multiple sub-steps:
  - Photoresist, expose photoresist to patterned light, dissolve weakened photoresist, expose chip surface to doping agent, dissolve all photoresist

## (1) Side view: P-type silicon



 
## (2) Put on photoresist


- The chip is immersed in a liquid chemical called photoresist, which coats the surface



 
### (3) Expose to light through mask (like a photographic negative)



 
(4) Immerse chip in a moderate solvent to remove the weakened photoresist



 (5) Expose chip to hot gaseous N-type doping agent; some atoms go into the substrate




 (6) Use a strong solvent to remove all the photoresist





 (7) Result: most of the chip surface is P-type,  
but a selected region is now N-type



# The big picture

- There are many Major Steps (change selected regions to N-type, put on insulator, put on metal layer, ...)
- Each Major Step requires a sequence of small steps: photoresist, mask, ...
- There may be over 100 steps
- But each step is helping to produce several billion transistors, all at once

# Refinements

- The manufacturing process has continually been refined. Example:
  - Some years ago, the feature size became smaller than the wavelength of visible light!
  - Solution: switch to X-rays rather than visible light
- These refinements are the reason Moore's Law has held for so long

# Dynamic Memory

# Dynamic Memory

An inverter can be used to store a bit:


- Connect the gate to either High or Low

This will either attract charge carriers into the channel, or it will release them allowing the channel to revert to its default type

- Then disconnect the gate

The state of the channel will stay the same, because of the capacitor effect

# Dynamic Register Bit

 

The stored bit is always available on *out*

When *ld* is High, the value of *x* (which must be strong) goes onto the gate of the memory bit. When *ld* then goes Low, this charge remains isolated (because of the capacitor effect) and the memory remains.

# Refresh

- An charge that is isolated on the gate of a pass transistor will **gradually dissipate**.
- Eventually, the gate will not have a strong enough charge to control the channel, and the register bit become unreadable.
- To prevent this, the bit must be **refreshed periodically**: the gate must be reconnected to power (low or high) to restore the stored charge to its full strength.

# Dynamic RAM


- In DRAM chips, the memory cells are organized as a matrix: a row of columns. The address is used to activate a column, and to select a row to choose the right bit.
- In addition to serving store and fetch requests, the DRAM also does a periodic refresh operation: each bit in a column is read out and put back



# Clock Signals


- A clock is a regular sequence of “ticks” that is broadcast globally.
- A clock value will be placed on the gates of pass transistors; during the interval that the clock is High, those transistors will be closed.

# The Two-Phase Clock

 

There are two distinct clock signals,  $\phi_1$  and  $\phi_2$ , which are never high simultaneously. (These can be generated from a single faster clock.)

# Dynamic Shift Register

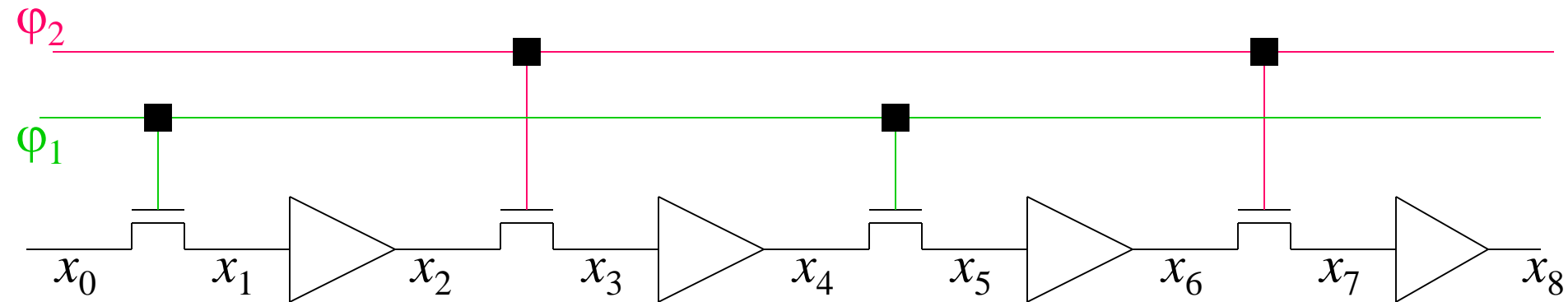

During  $\phi_1$


$$\begin{aligned} x_1 &= x_0, & x_2 &= x_1 \\ x_5 &= x_4, & x_6 &= x_5 \end{aligned}$$

During  $\phi_2$

$$\begin{aligned} x_3 &= x_2, & x_4 &= x_3 \\ x_7 &= x_6, & x_8 &= x_7 \end{aligned}$$

This circuit consists entirely of combinational components, with no feedback. Yet it has state, and it implements a shift register!

# Initial State, with Clocks Low

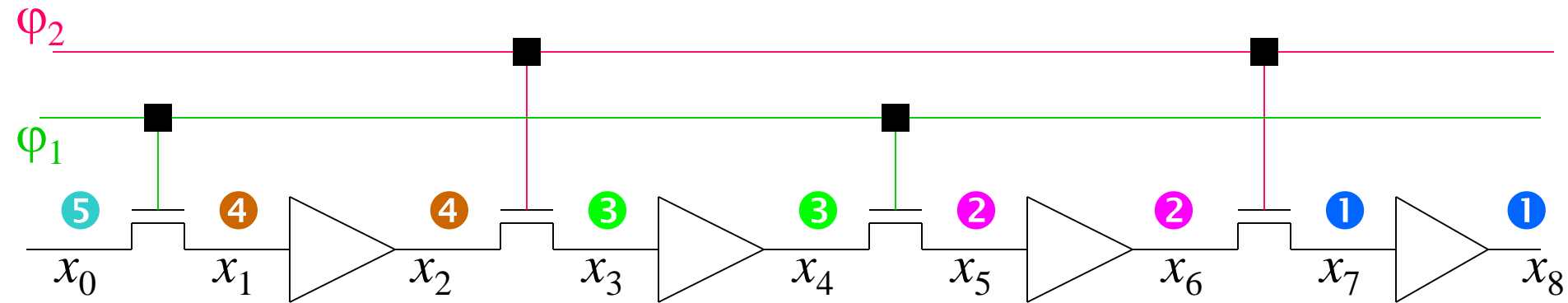

## During $\phi_1$


$$\begin{aligned} x_1 &= x_0, & x_2 &= x_1 \\ x_5 &= x_4, & x_6 &= x_5 \end{aligned}$$

## During $\phi_2$

$$\begin{aligned} x_3 &= x_2, & x_4 &= x_3 \\ x_7 &= x_6, & x_8 &= x_7 \end{aligned}$$

The charge on the gate  $x_3$  is isolated, so the value of  $x_3$  remains steady with value **3**. This also causes the buffer to keep the restored signal  $x_4$  steady. Similarly,  $x_1$ — $x_2$ ,  $x_5$ — $x_6$ , and  $x_7$ — $x_8$  remain steady.

# Step 1: Clock $\phi_1$ High

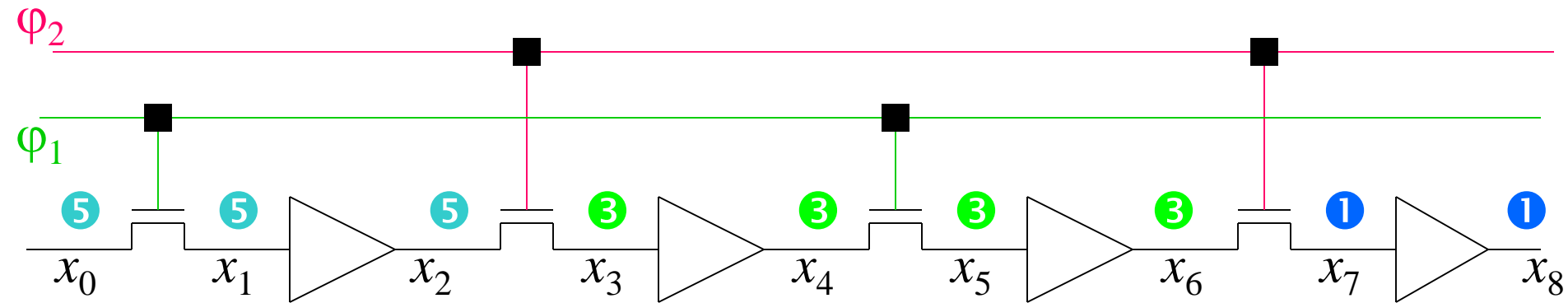

During  $\phi_1$


$$\begin{aligned}x_1 &= x_0, & x_2 &= x_1 \\x_5 &= x_4, & x_6 &= x_5\end{aligned}$$

During  $\phi_2$

$$\begin{aligned}x_3 &= x_2, & x_4 &= x_3 \\x_7 &= x_6, & x_8 &= x_7\end{aligned}$$

The value **5** moves onto  $x_1$  and then  $x_2$ , destroying the old value **4**. Similarly, **3** moves onto  $x_5$  and  $x_6$ , destroying **2**, and it remains unaffected on  $x_3$ — $x_4$ , since  $x_3$  is still isolated.

## Step 2: Clock $\phi_2$ High

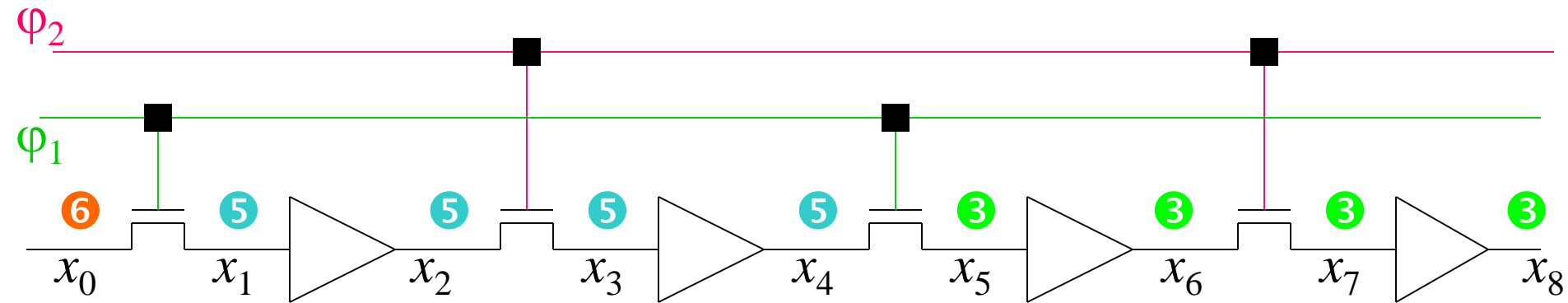

During  $\phi_1$


$$\begin{aligned} x_1 &= x_0, & x_2 &= x_1 \\ x_5 &= x_4, & x_6 &= x_5 \end{aligned}$$

The value **5** moves up to  $x_3$  and then  $x_4$ , and **3** moves onto  $x_7$  and  $x_8$ . A new input **6** is arriving.

During  $\phi_2$

$$\begin{aligned} x_3 &= x_2, & x_4 &= x_3 \\ x_7 &= x_6, & x_8 &= x_7 \end{aligned}$$

## Step 3: Clock $\phi_1$ High

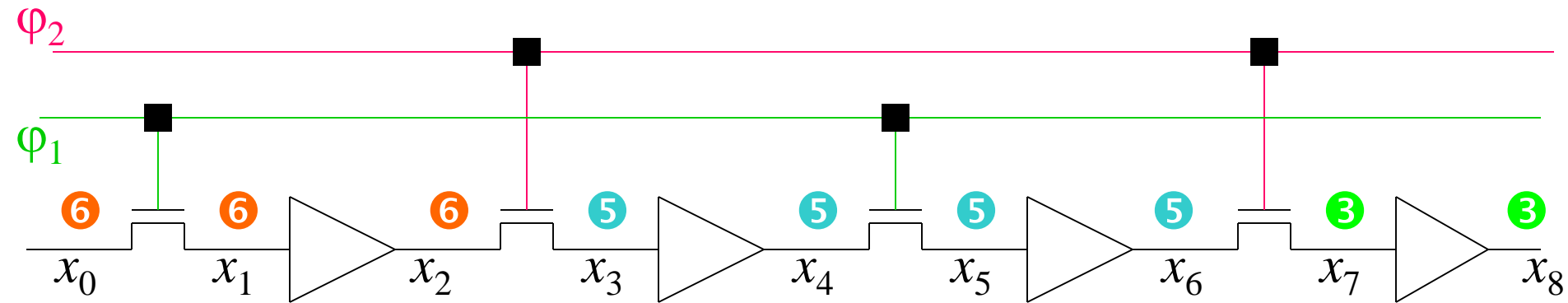

During  $\phi_1$

$$x_1 = x_0, \quad x_2 = x_1$$

$$x_5 = x_4, \quad x_6 = x_5$$


All the data values are moving along...

During  $\phi_2$

$$x_3 = x_2, \quad x_4 = x_3$$

$$x_7 = x_6, \quad x_8 = x_7$$

## Step 4: Clock $\varphi_2$ High

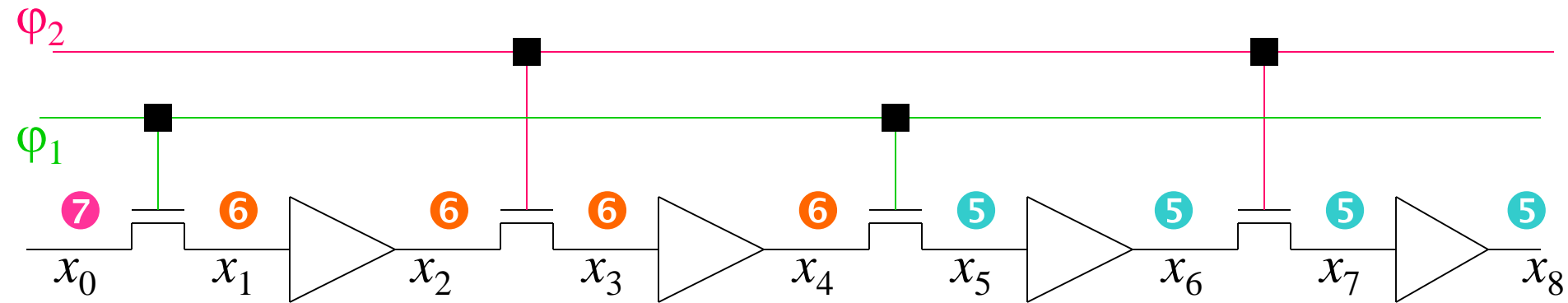

During  $\varphi_1$

$$x_1 = x_0, \quad x_2 = x_1$$

$$x_5 = x_4, \quad x_6 = x_5$$

All the data values are moving along... and the new input **7** is arriving.

During  $\varphi_2$

$$x_3 = x_2, \quad x_4 = x_3$$


$$x_7 = x_6, \quad x_8 = x_7$$



# Pseudo-static Register Bit

- Use capacitor to store the bit, as in shift register – it is fundamentally a dynamic memory device.
- The bit value is refreshed regularly by recirculation, similarly to the dynamic shift register.

# Pseudo-Static Register Cell

 


# Decay, Refresh, and Feedback

- The quality of a stored bit will **decay** gradually
- Therefore, all electronic forms of memory require some sort of **refresh** (static, dynamic, pseudo-static, shift-register, ...)
- This is achieved using **feedback**: the bit must be read out while it's still readable, and a restoring logic device must then put the bit back in full strength

# Physical and Abstract Clock

Physical clock—usually multiple phases

 

Time →

Abstract clock

Clock ticks

# Circuit diagram

<https://xkcd.com/730/>

